

Pre Lab 1

Y CD	AB			
	00	01	11	10
00	X	0	1	1
01	1	1	X	0
11	1	1	X	0
10	0	0	X	1

$$Y = \bar{A}D + A\bar{D}$$